

Roth and John 3rd edition – Chapters 3 and 6 (Sections 6.1 & 6.2)

Note: [Equivalent problems from the 2nd edition are specified in brackets.]

1. Problem 3.1 [3.1]

- **Note:** Give an exact answer including the size of the ROM memory, and specify reasoning for it.
- **Example 3.1 (a):** $2^{17} \times 9$ because there are 8 input bits for each input to the adder, so $2 \times 8 = 16$ bits, plus an additional input bit for the Cin, for a total of 17 input bits. The adder produces 8 sum output bits and 1 Cout, for a total of 9 output bits. We need a truth table (ROM implementation) with 2^{17} rows, and 9 columns, therefore $2^{17} \times 9$ bits are needed for the ROM realization of a 8-bit full adder with a carry in.

2. Problem 3.10 (Part a) [3.3 (a)]

3. Problem 3.19 [3.12]

4. Problem 3.20 [3.13]

5. Problem 6.5 [6.5]

- Note: You can cut and paste the images from the following page and use them to draw the appropriate connections (rather than redrawing the figures yourself)

6. Repeat steps a-d of problem 6.5, but design a 2-bit full-adder.



- Inputs: A1, A0, B1, B0, Cin. Outputs: S1, S0, Cout. Additionally, map the solution using only 5-input look-up tables; show the contents of the tables.


7. Problem 6.10 [No 2nd edition equivalent, problem is specified below]

a) How many LUT3 are required to create the following function?

$$F_1 = W + X'Z + WY + WZ' + X'Z'$$

b) Give the content of the LUTs

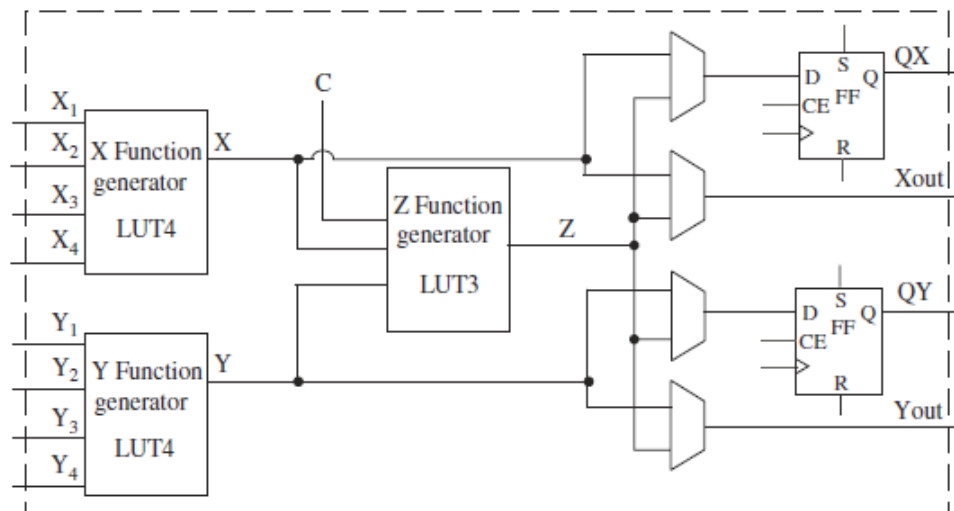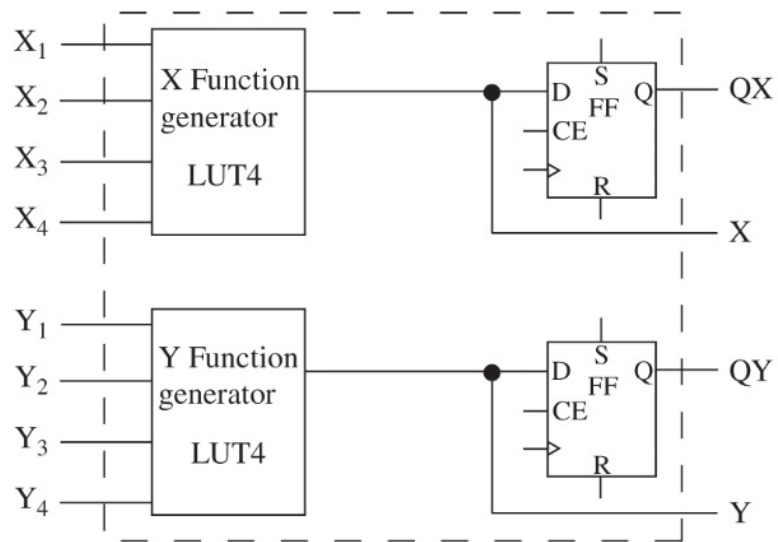

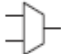 = Programmable MUX